

Chapter 17 Two-Port Networks

User Note:

Run **View Show**
under the **Slide Show**
menu to
enable slide
selection.


- Fig. 17.1 (a) A one-port network.
- Fig. 17.5 A general two-port with terminal voltages and currents...
- Fig. 17.6 Circuit for Example 17.4.
- Fig. 17.9 (a,b) Two-ports which are equivalent to any general ...
- Fig. 17.10 The three-terminal Δ network (a) and the three-terminal...
- Fig. 17.11 Circuit for Example 17.6.
- Table 17.1 Transformations between y, z, h, and t parameters.

W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.


Copyright ©2002 McGraw-Hill. All rights reserved.

A one-port network:

Equivalente Thevenin y/o Eq. Norton

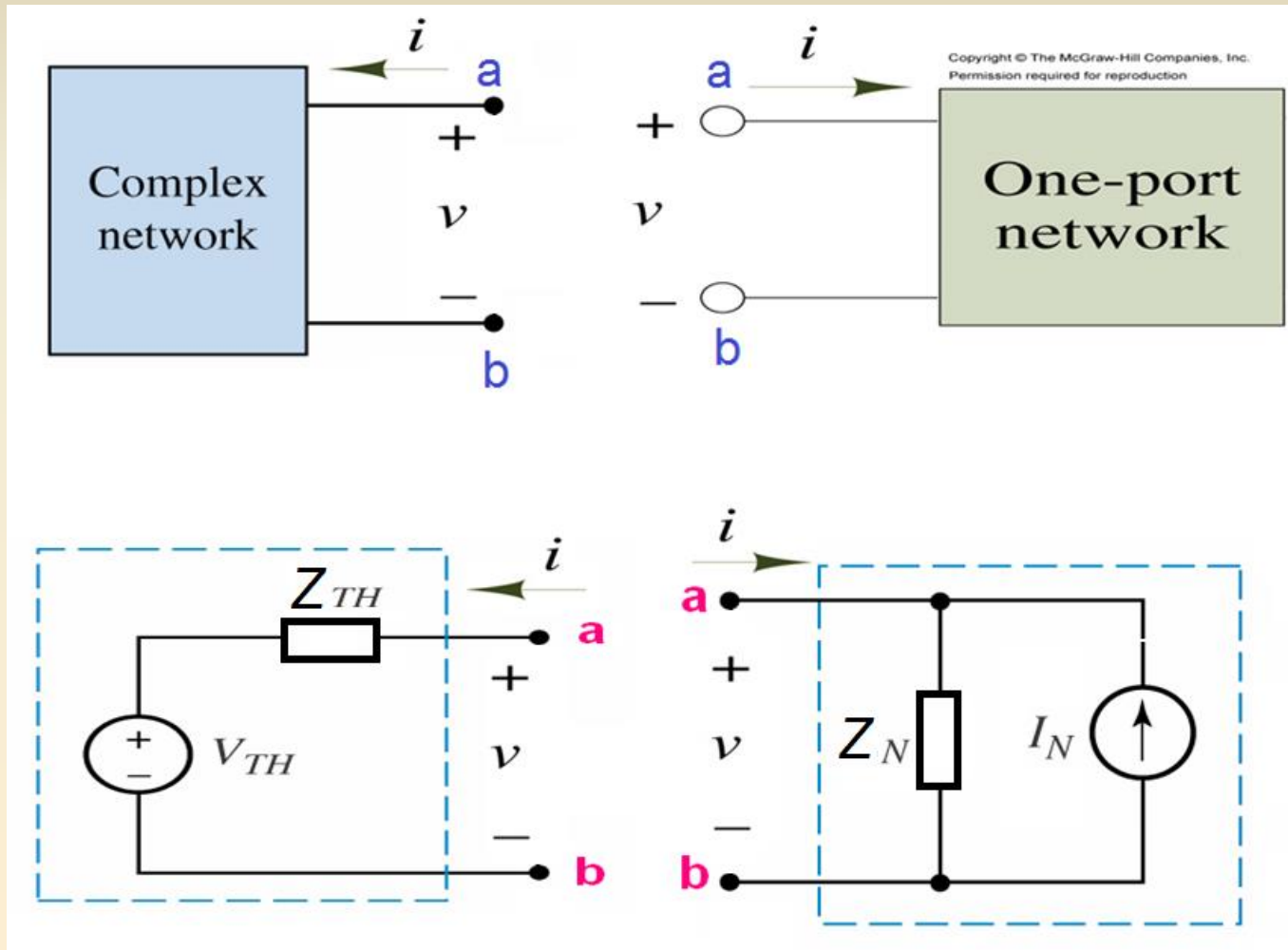

A two port network.

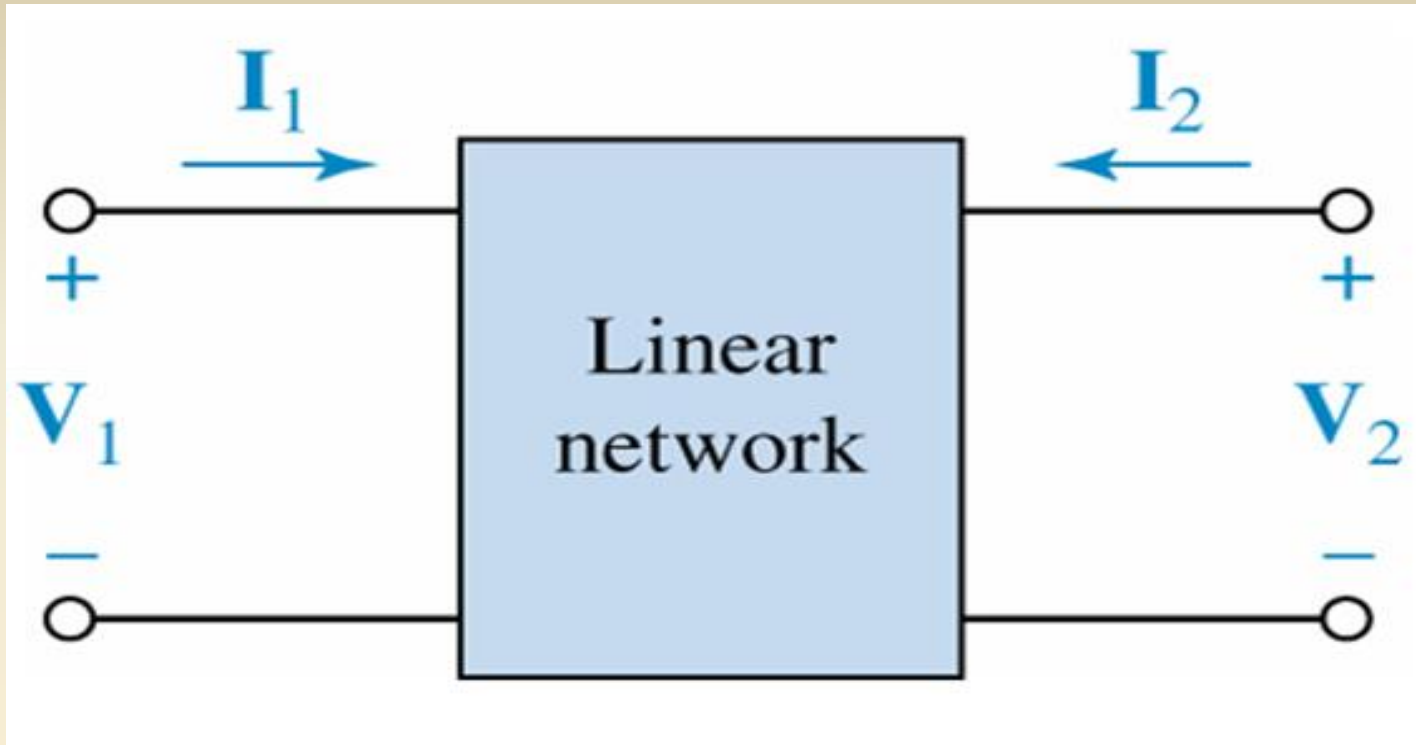

A general **two-port** with terminal voltages and currents specified. The two-port is composed of linear elements, possibly including dependent sources, but not containing any independent sources.

W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.

Copyright ©2002 McGraw-Hill. All rights reserved.

Ecuaciones que describen una red bipuerto:

$$Q_1 = K_{11}P_1 + K_{12}P_2$$

$$Q_2 = K_{21}P_1 + K_{22}P_2$$


$$\Rightarrow \begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \end{bmatrix}$$

Caso	Q_1	Q_2	P_1	P_2	Tipo de Parámetros
1	V_1	V_2	I_1	I_2	Z : Impedancia o ckto abierto (OC)
2	I_1	I_2	V_1	V_2	Y : Admitancia o corto ckto (SC)
3	I_1	V_2	V_1	I_2	q : Híbridos inversos
4	V_1	I_2	I_1	V_2	h : Híbridos
5	V_1	I_1	V_2	I_2	t : ABCD o Transmisión
6	V_2	I_2	V_1	I_1	T' : \overline{ABCD} o Transmisión inversos

Caso 1: Parámetros “Z” o de circuito abierto:

$$\begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \end{bmatrix} \Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

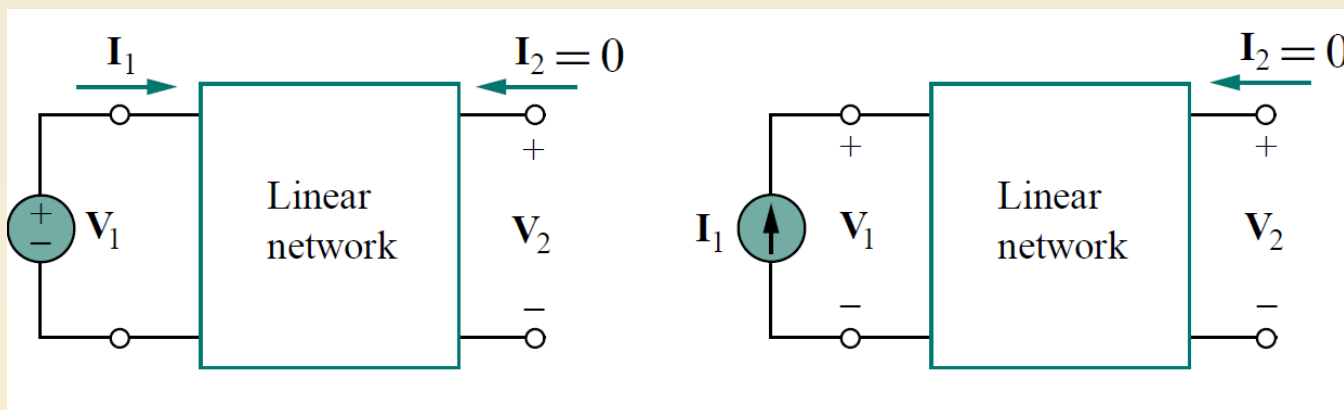haciendo $I_2 = 0$: (puerta₂ en ckto abierto)




$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \Rightarrow Z_{in} \text{ puerta}_1 \text{ con puerta}_2 \text{ abierta}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \Rightarrow \text{trans_impedancia}_{21} \text{ a puerta}_2 \text{ abierta}$$

Caso 1: Parámetros “Z” o de circuito abierto:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

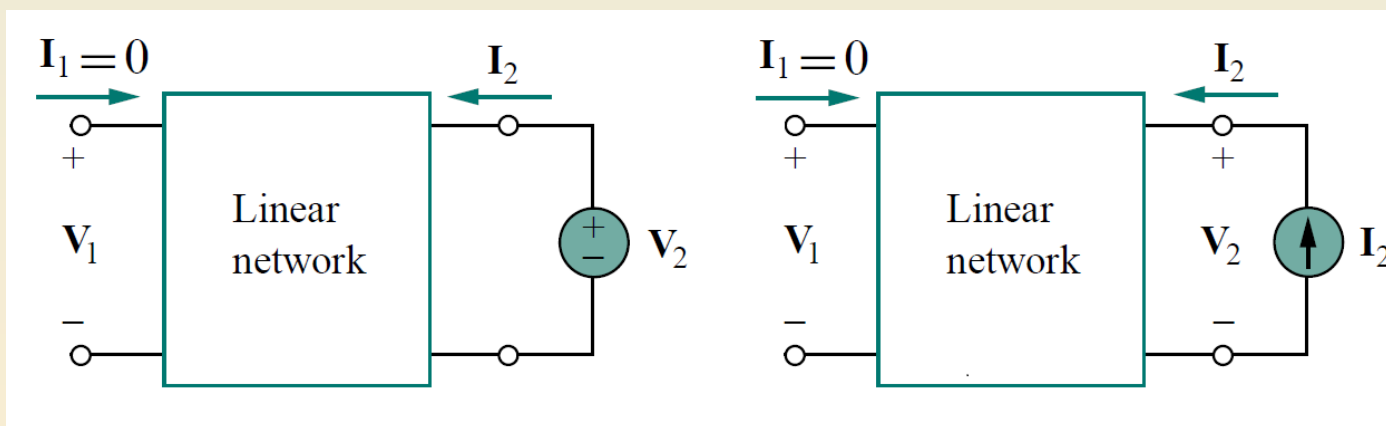haciendo $I_1 = 0$: (puerta $_1$ en ckto abierto)





$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \Rightarrow \text{trans_impedancia}_{12} \text{ a puerta } _1 \text{ en ckto abierto}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \Rightarrow Z_{in} \text{ puerta } _2 \text{ con puerta } _1 \text{ abierta}$$

Caso 1: Parámetros “Z” o circuito abierto: Red bipuerto equivalente (\approx doble thevenin)


$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

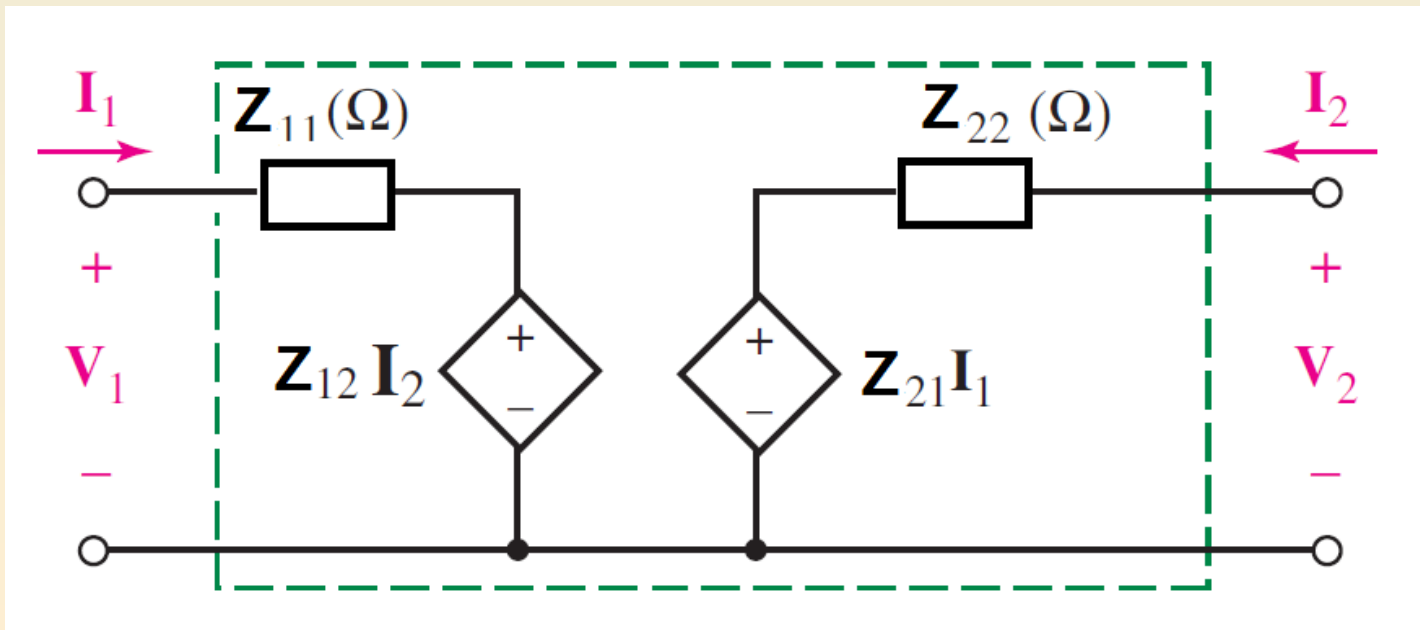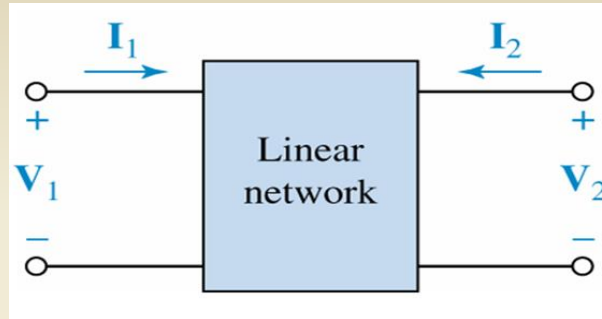

Caso 2: Parámetros “Y” o de corto circuito:

$$\begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

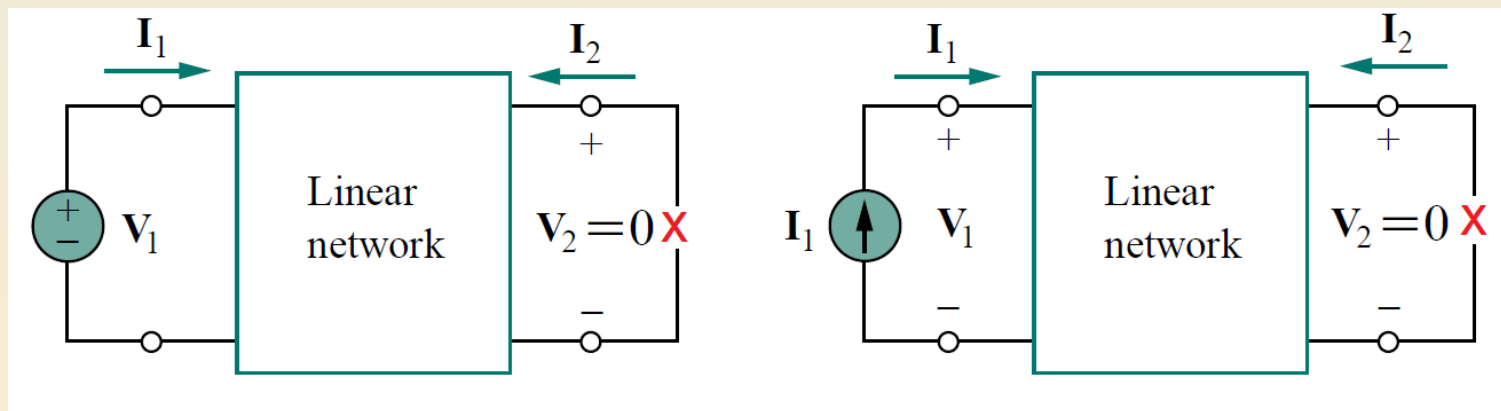haciendo $V_2 = 0$: (puerta₂ en corto ckto)




$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \Rightarrow Y_{in} \text{ puerta}_1 \text{ con puerta}_2 \text{ en corto ckto.}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \Rightarrow \text{trans_admitancia}_{21} \text{ a puerta}_2 \text{ en corto}$$

Caso 2: Parámetros “Y” o de corto circuito:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


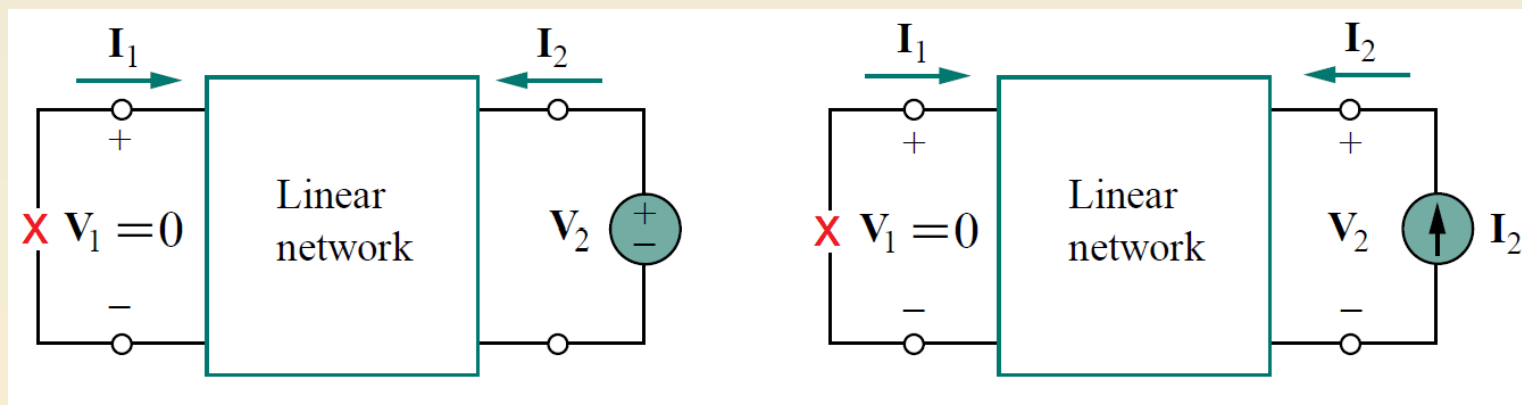
haciendo $V_1 = 0$: (puerta₁ en corto ckto)



$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \Rightarrow \text{trans_admitancia}_{12} \text{ a puerta}_1 \text{ en corto ckto}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \Rightarrow Y_{in} \text{ puerta}_2 \text{ con puerta}_1 \text{ en corto ckto.}$$


Caso 2: Parámetros “Y” o corto ckto: Red bipuerto equivalente (\approx doble norton)

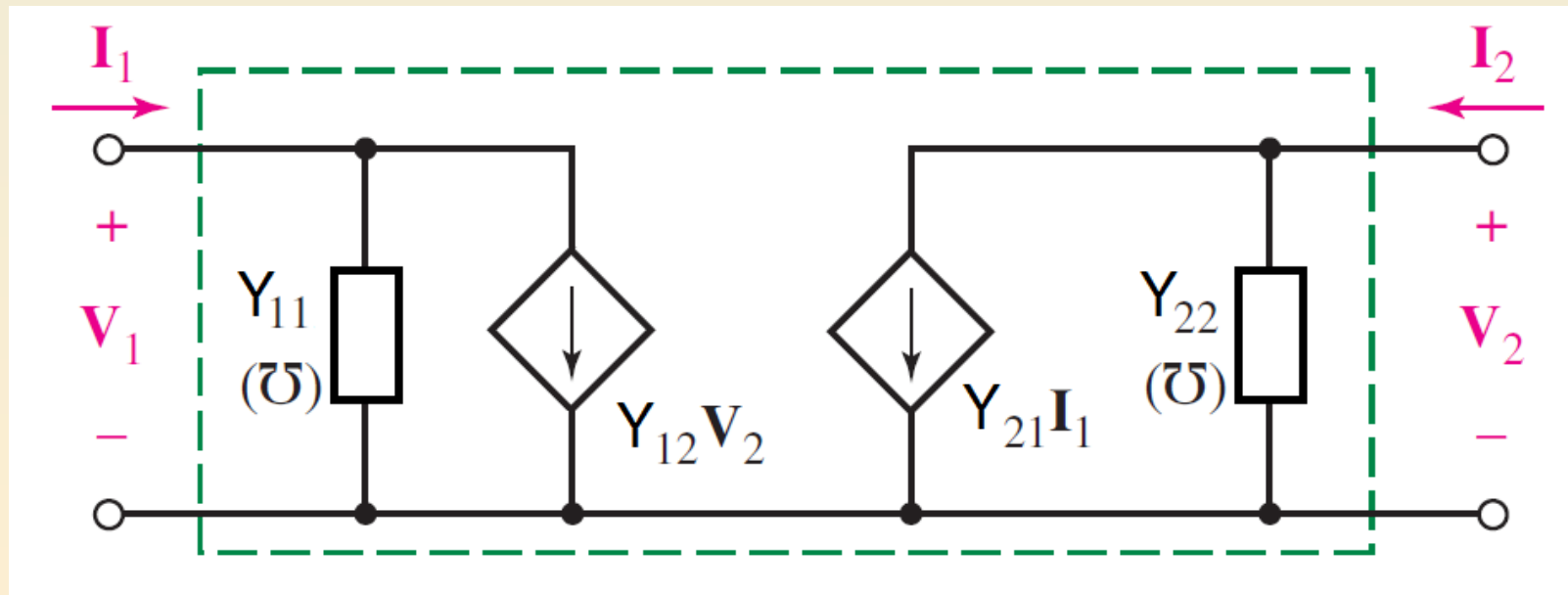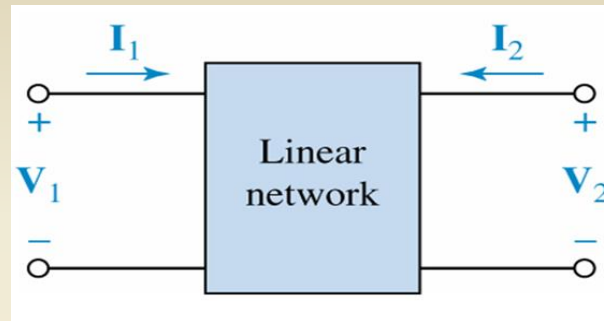

Caso 3: Parámetros “q” o híbridos inversos:

$$\begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} q_{11} & q_{12} \\ q_{21} & q_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

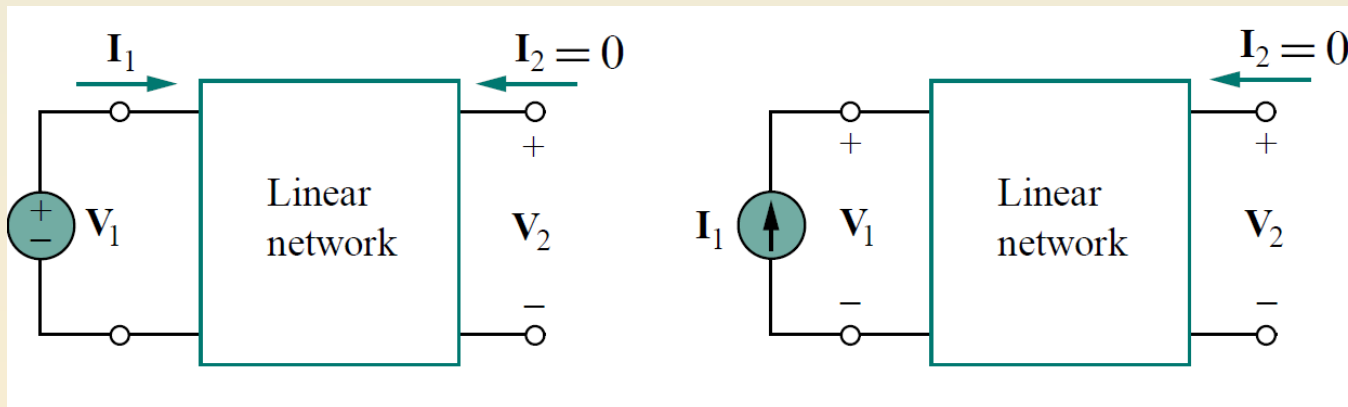haciendo $I_2 = 0$: (puerta₂ en ckto abierto)




$$q_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \Rightarrow Y_{in} \text{ puerta}_1 \text{ con puerta}_2 \text{ abierta}$$

$$q_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \Rightarrow \text{gain tensión a puerta}_2 \text{ abierta}$$

Caso 3: Parámetros “q” o híbridos inversos:

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} q_{11} & q_{12} \\ q_{21} & q_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$


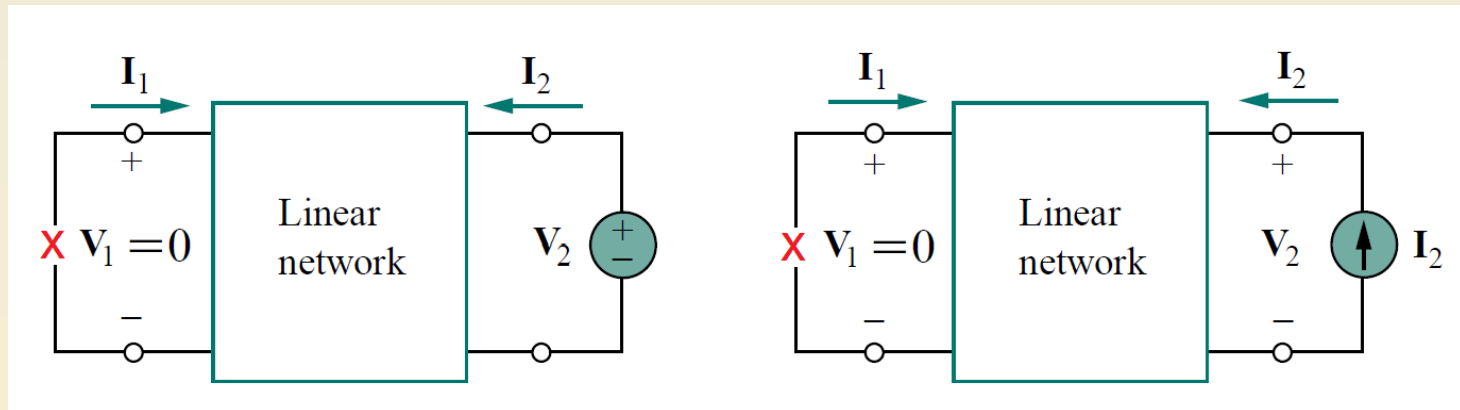
haciendo $V_1 = 0$: (puerta₁ en corto ckto)



$$q_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} \Rightarrow \text{gain inversa de corriente a puerta}_1 \text{ en corto ckto}$$

$$q_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} \Rightarrow Z_{in} \text{ puerta}_2 \text{ con puerta}_1 \text{ en corto ckto}$$


Caso 3: Parámetros “ q ” o híbridos inversos: Red bipuerto equivalente (\approx norton+thevenin)

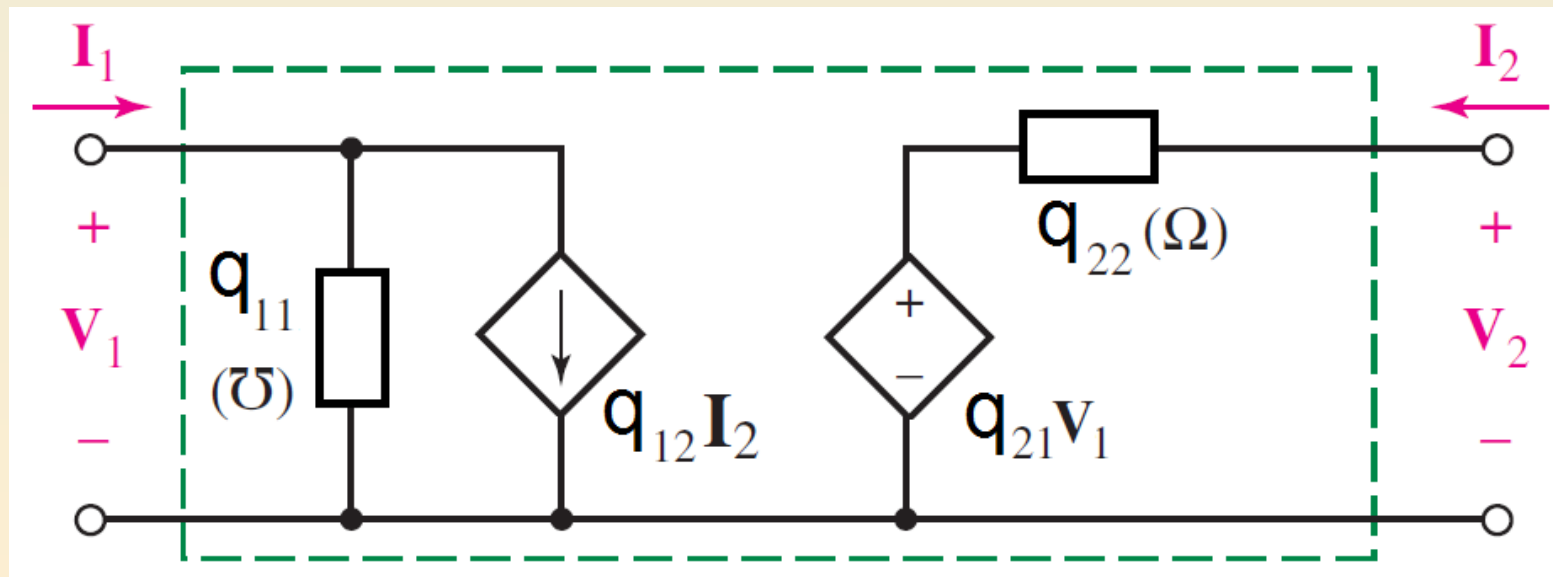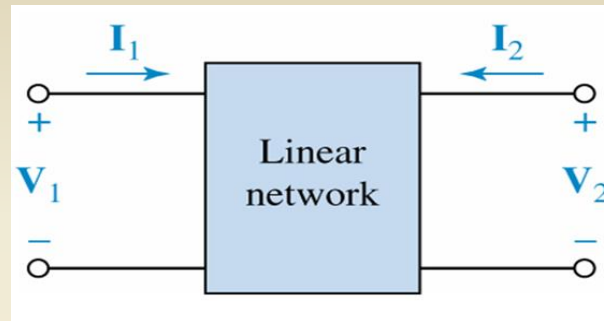

Caso 4: Parámetros “h” o híbridos:

$$\begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \end{bmatrix} \Rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

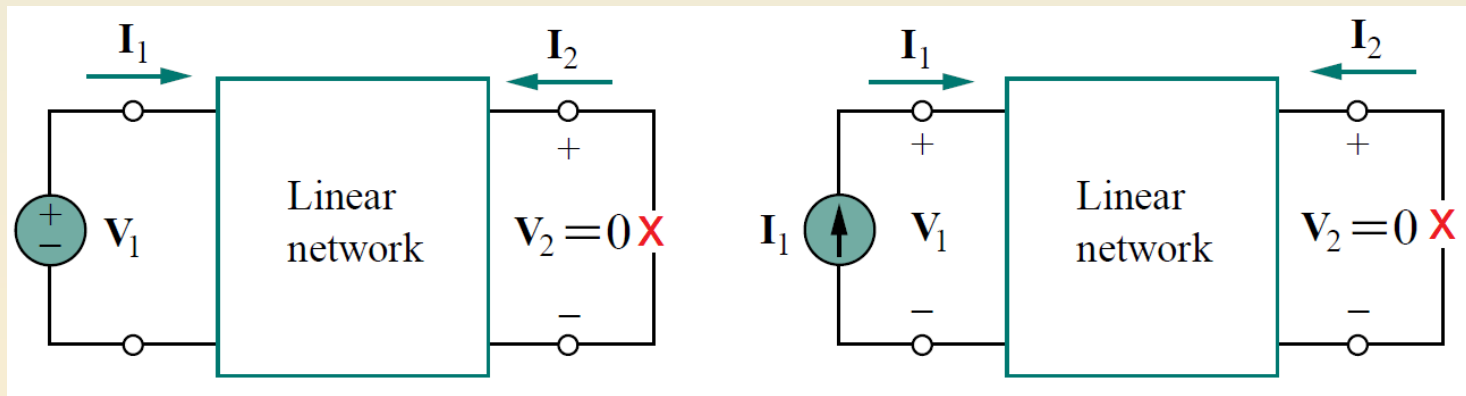haciendo $V_2 = 0$: (puerta₂ en corto ckto)




$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \Rightarrow Z_{in} \text{ puerta}_1 \text{ con puerta}_2 \text{ en corto ckto}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \Rightarrow \text{gain de corriente a puerta}_2 \text{ en corto ckto}$$

Caso 4: Parámetros “h” o híbridos:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


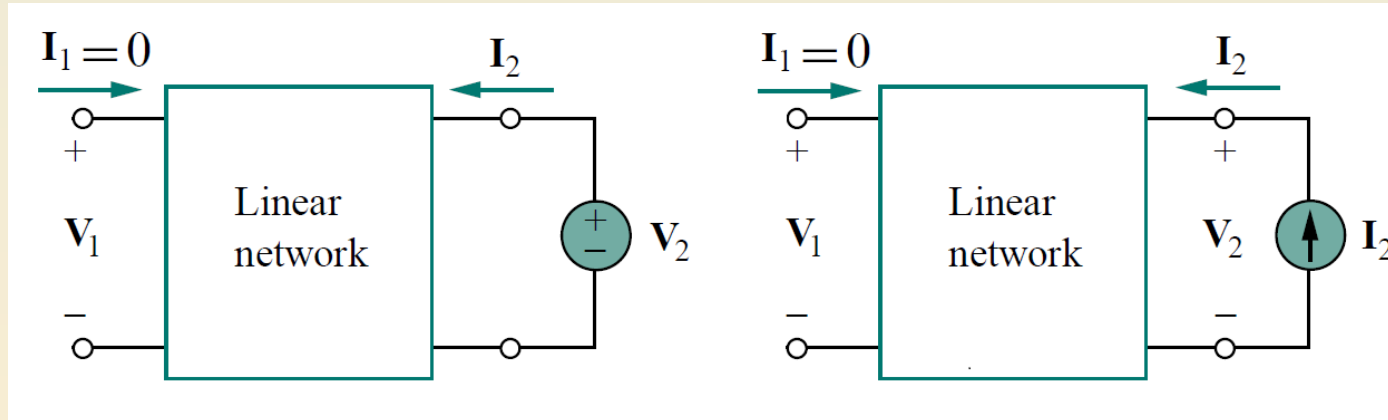
haciendo $I_1 = 0$: (puerta₁ en ckto abierto)



$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \Rightarrow \text{gain inversa de tensión a puerta}_1 \text{ abierta}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \Rightarrow Z_{in} \text{ puerta}_2 \text{ con puerta}_1 \text{ abierta}$$

Caso 4: Parámetros “h” o híbridos: Red bipuerto equivalente (\approx thevenin+norton)

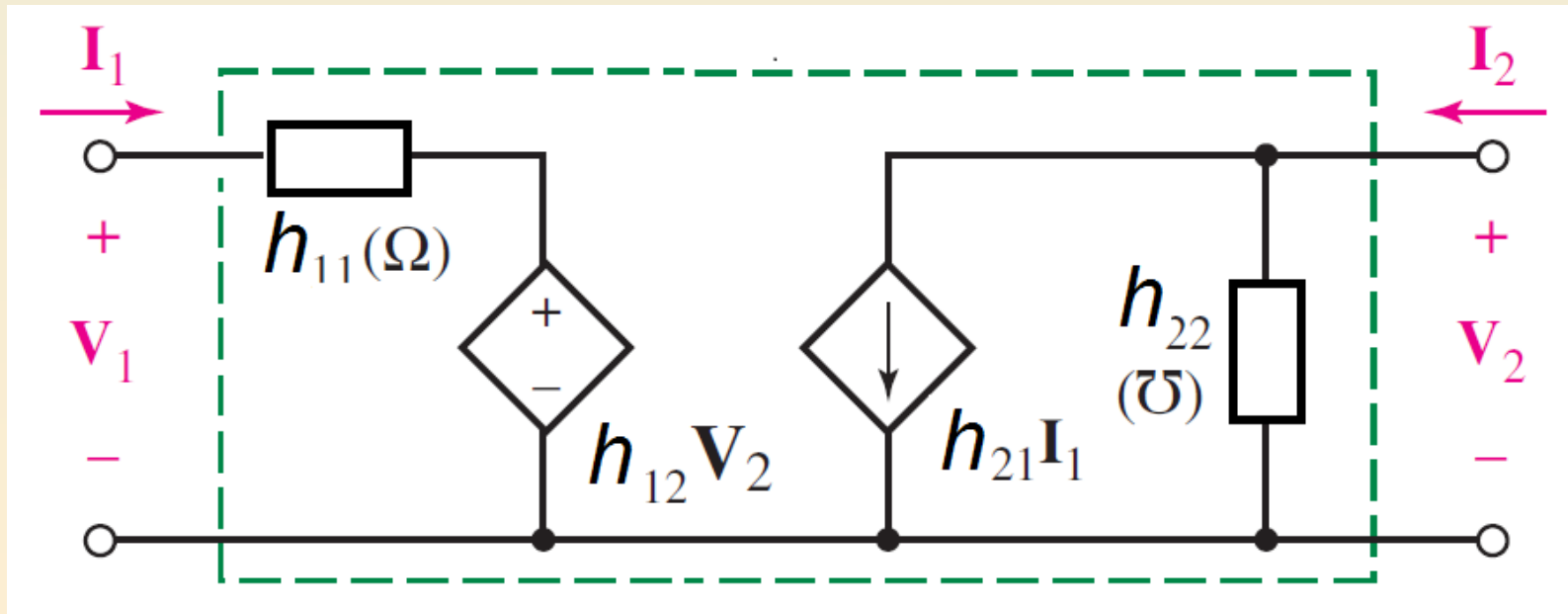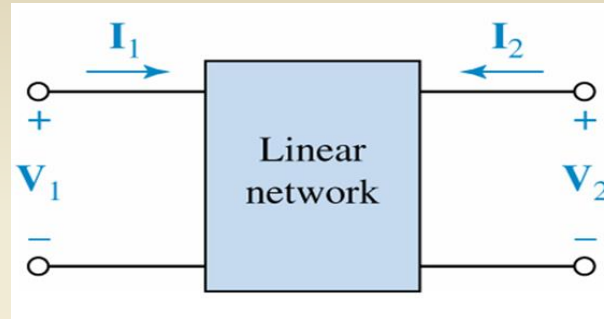

Caso 5: Parámetros “t” o “ABCD” o transmisión:

$$\begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \end{bmatrix} \Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

haciendo $I_2 = 0$: (puerta₂ abierta)

$$t_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0} = A \Rightarrow \text{gain inversa de tension con puerta}_2 \text{ abierta}$$

$$t_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} = C \Rightarrow \text{trans_admitancia}_{21} \text{ a puerta}_2 \text{ abierta}$$

haciendo $V_2 = 0$: (puerta₂ en corto ckto)

$$t_{12} = \left. \frac{V_1}{I_2} \right|_{V_2=0} = B \Rightarrow \text{trans_impedancia}_{12} \text{ con puerta}_2 \text{ en corto ckto}$$

$$t_{22} = \left. \frac{I_1}{I_2} \right|_{V_2=0} = D \Rightarrow \text{gain inversa de corriente con puerta}_2 \text{ en corto ckto}$$

Caso 6: Parámetros “ T ” o “ $ABCD$ ” o transmisión inversos:

$$\begin{bmatrix} Q_1 \\ Q_2 \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \end{bmatrix} \Rightarrow \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

haciendo $I_1 = 0$: (puerta₁ en ckto abierto)

$$T_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0} = a \Rightarrow \text{gain de tension con puerta}_1 \text{ abierta}$$

$$T_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0} = c \Rightarrow \text{trans_admitancia}_{21} \text{ a puerta}_1 \text{ abierta}$$

haciendo $V_1 = 0$: (puerta₁ en corto ckto)

$$T_{12} = \left. \frac{V_2}{I_1} \right|_{V_1=0} = b \Rightarrow \text{transimpedancia}_{12} \text{ a puerta}_1 \text{ en corto ckto}$$

$$T_{22} = \left. \frac{I_2}{I_1} \right|_{V_1=0} = d \Rightarrow \text{gain corriente con puerta}_1 \text{ en corto ckto}$$

TABLE 18.1 Conversion of two-port parameters.


	z		y		h		g		T		t	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{1}{g_{11}}$	$-\frac{g_{12}}{g_{11}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$	$\frac{d}{c}$	$\frac{1}{c}$
	z_{21}	z_{22}	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{g_{21}}{g_{11}}$	$\frac{\Delta_g}{g_{11}}$	$\frac{1}{C}$	$\frac{D}{C}$	$\frac{\Delta_t}{c}$	$\frac{a}{c}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{\Delta_g}{g_{22}}$	$\frac{g_{12}}{g_{22}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$	$\frac{a}{b}$	$-\frac{1}{b}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{g_{21}}{g_{22}}$	$\frac{1}{g_{22}}$	$-\frac{1}{B}$	$\frac{A}{B}$	$-\frac{\Delta_t}{b}$	$\frac{d}{b}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{g_{22}}{\Delta_g}$	$-\frac{g_{12}}{\Delta_g}$	$\frac{B}{D}$	$\frac{\Delta_T}{D}$	$\frac{b}{a}$	$\frac{1}{a}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$-\frac{g_{21}}{\Delta_g}$	$\frac{g_{11}}{\Delta_g}$	$-\frac{1}{D}$	$\frac{C}{D}$	$\frac{\Delta_t}{a}$	$\frac{c}{a}$
g	$\frac{1}{z_{11}}$	$-\frac{z_{12}}{z_{11}}$	$\frac{\Delta_y}{y_{22}}$	$\frac{y_{12}}{y_{22}}$	$\frac{h_{22}}{\Delta_h}$	$-\frac{h_{12}}{\Delta_h}$	g_{11}	g_{12}	$\frac{C}{A}$	$-\frac{\Delta_T}{A}$	$\frac{c}{d}$	$-\frac{1}{d}$
	$\frac{z_{21}}{z_{11}}$	$\frac{\Delta_z}{z_{11}}$	$-\frac{y_{21}}{y_{22}}$	$\frac{1}{y_{22}}$	$-\frac{h_{21}}{\Delta_h}$	$\frac{h_{11}}{\Delta_h}$	g_{21}	g_{22}	$\frac{1}{A}$	$\frac{B}{A}$	$\frac{\Delta_t}{d}$	$-\frac{b}{d}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$-\frac{h_{11}}{h_{21}}$	$\frac{1}{g_{21}}$	$\frac{g_{22}}{g_{21}}$	A	B	$\frac{d}{\Delta_t}$	$\frac{b}{\Delta_t}$
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$-\frac{1}{h_{21}}$	$\frac{g_{11}}{g_{21}}$	$\frac{\Delta_g}{g_{21}}$	C	D	$\frac{c}{\Delta_t}$	$\frac{a}{\Delta_t}$
	$\frac{z_{22}}{z_{12}}$	$\frac{\Delta_z}{z_{12}}$	$-\frac{y_{11}}{y_{12}}$	$-\frac{1}{y_{12}}$	$\frac{1}{h_{12}}$	$\frac{h_{11}}{h_{12}}$	$-\frac{\Delta_g}{g_{12}}$	$-\frac{g_{22}}{g_{12}}$	$\frac{D}{\Delta_T}$	$\frac{B}{\Delta_T}$	a	b
t	$\frac{1}{z_{12}}$	$\frac{z_{11}}{z_{12}}$	$-\frac{\Delta_y}{y_{12}}$	$-\frac{y_{22}}{y_{12}}$	$\frac{h_{22}}{h_{12}}$	$\frac{\Delta_h}{h_{12}}$	$-\frac{g_{11}}{g_{12}}$	$-\frac{1}{g_{12}}$	$\frac{C}{\Delta_T}$	$\frac{A}{\Delta_T}$	c	d

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21}, \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21}, \quad \Delta_T = AD - BC$$

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21}, \quad \Delta_g = g_{11}g_{22} - g_{12}g_{21}, \quad \Delta_t = ad - bc$$

Teorema de Reciprocidad:

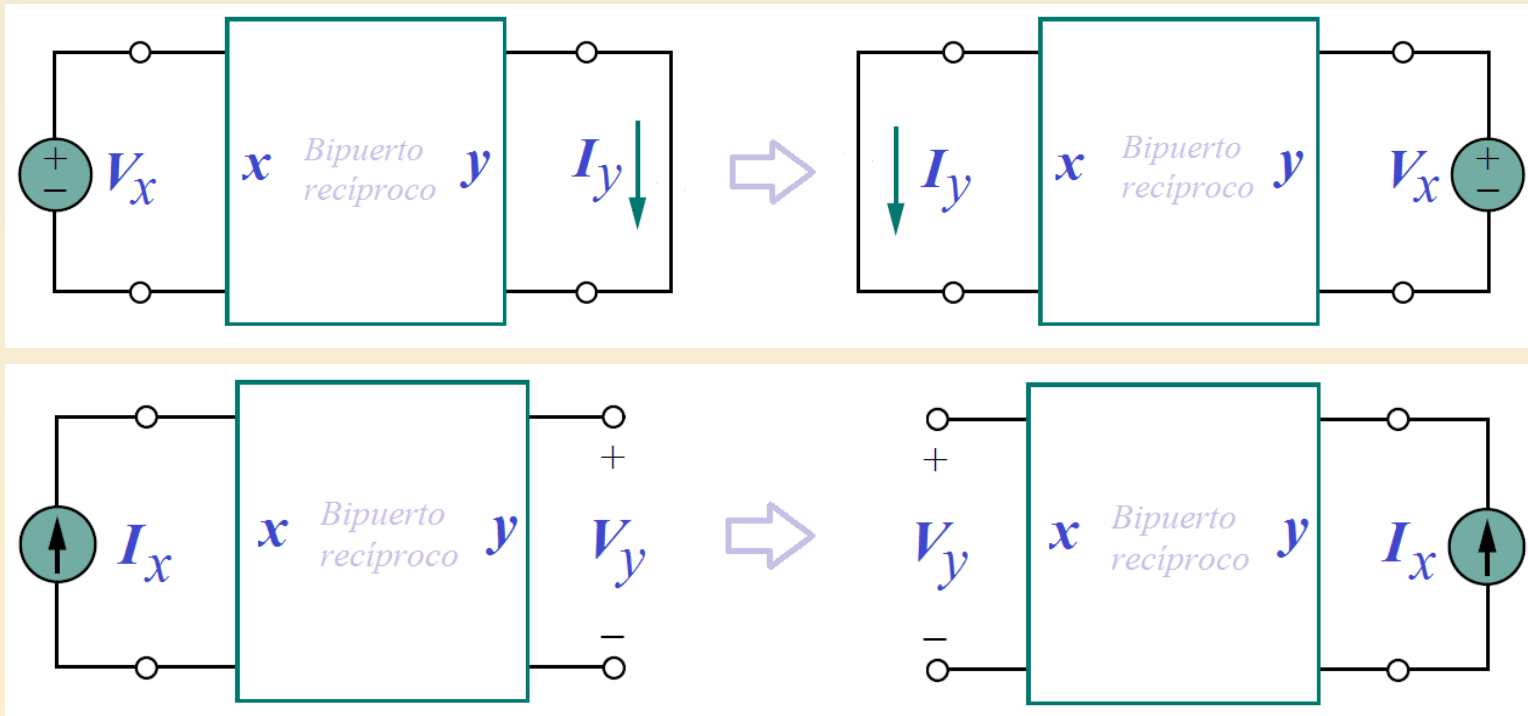En cualquier red de dos puertos recíproca, si la única fuente de tensión V_x en la rama “x” produce una respuesta de corriente I_y en la rama “y”, entonces, al intercambiar la fuente de tensión de la rama “x” y colocarla en la rama “y”, producirá la misma respuesta de corriente I_y pero en la rama “x”



Reciporcidad:

Una red bipuertos es recíproca si cumple las siguientes condiciones:

a) $Z_{12} = Z_{21}$


b) $Y_{12} = Y_{21}$

c) $h_{12} = -h_{21}$

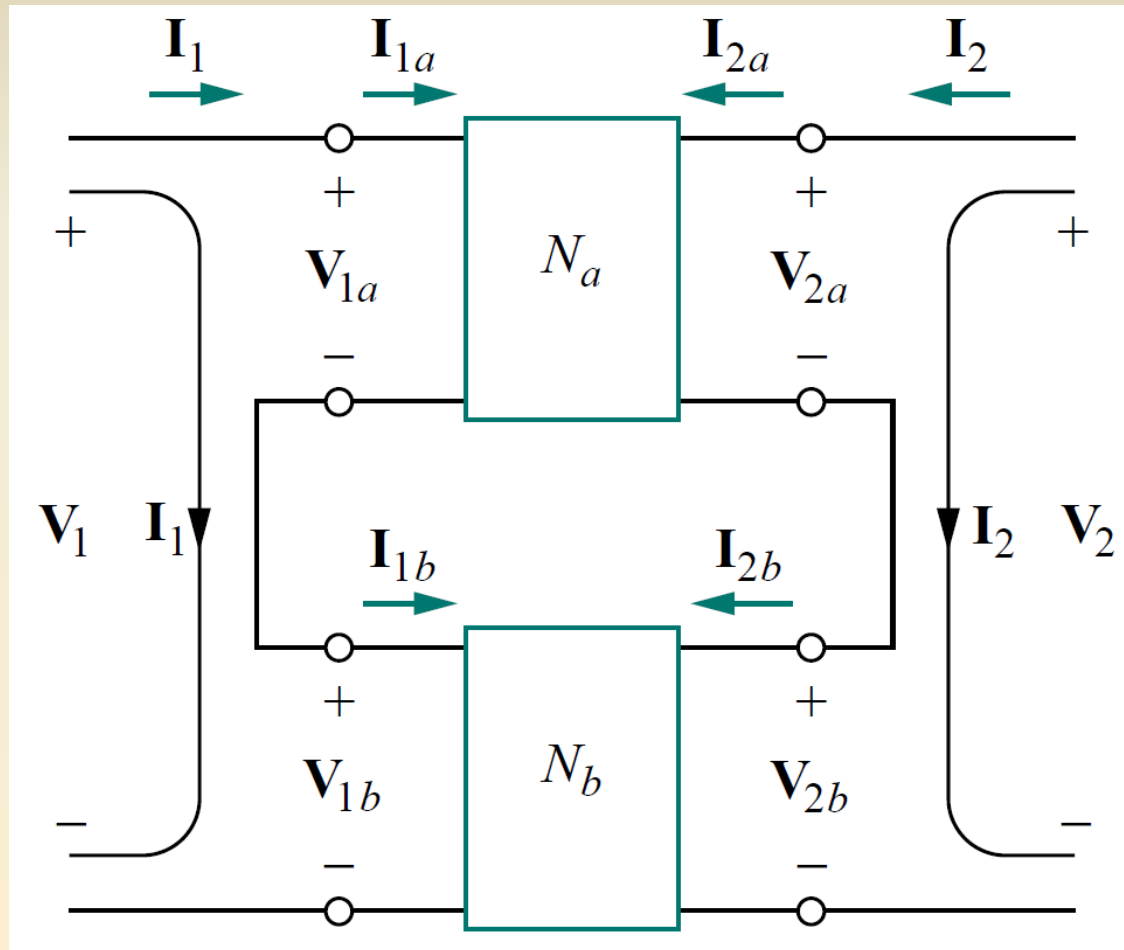
d) $AD - BC = 1$

Cuando $Z_{11} = Z_{22}$ la red se considera simétrica:
2 mitades similares.


Interconexión de Bipuertos: Arreglo Serie:



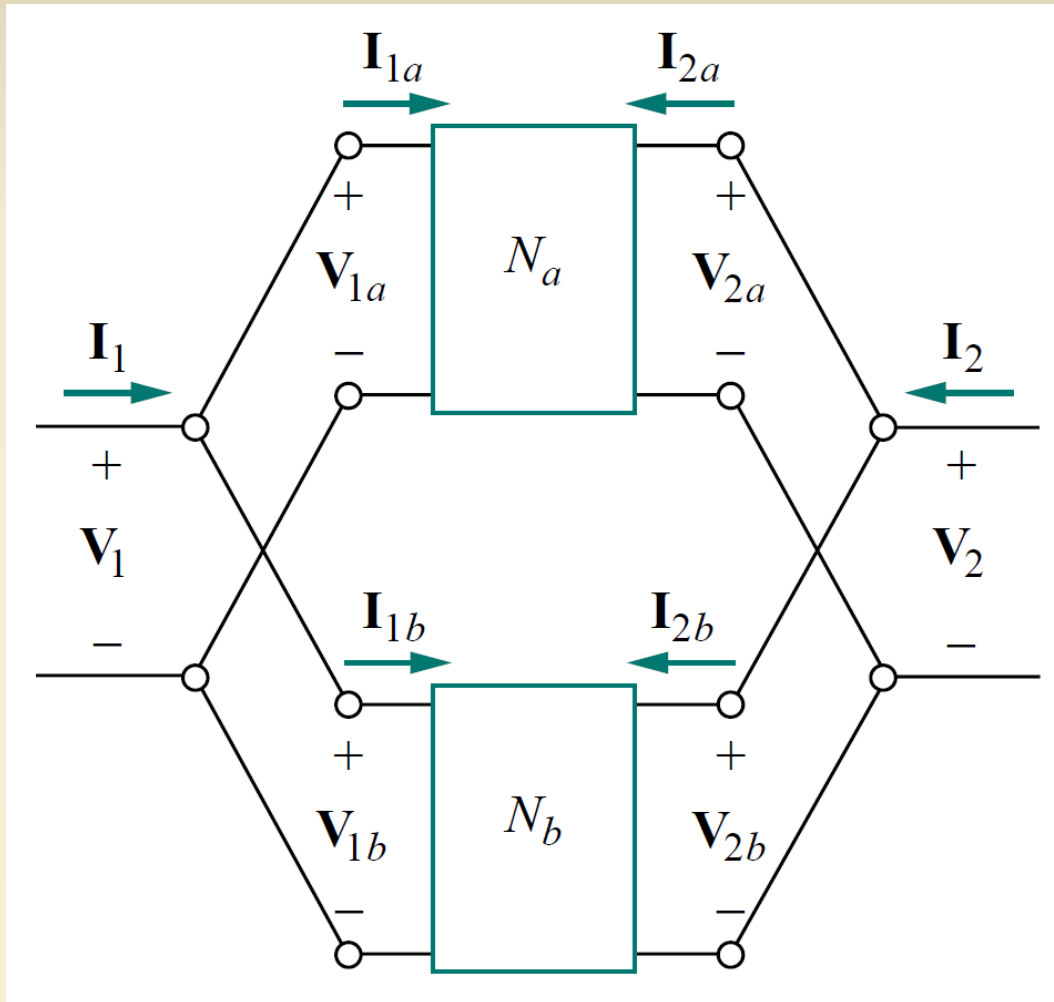
Interconexión de Bipuertos: Arreglo Paralelo:




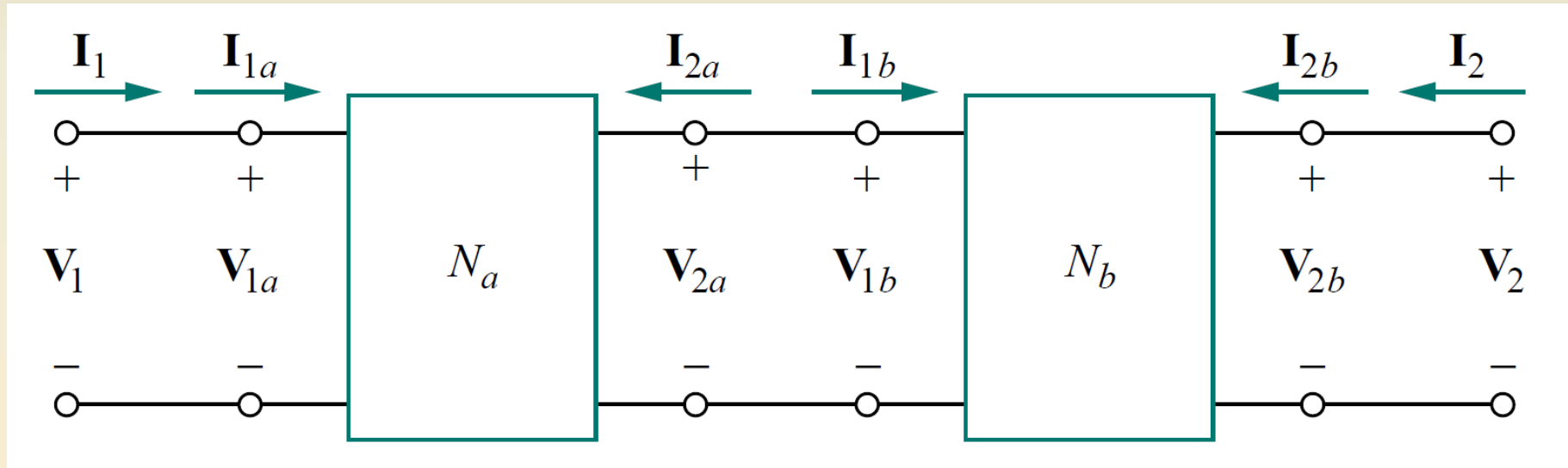Interconexión de Bipuertos: Arreglo en Cascada:



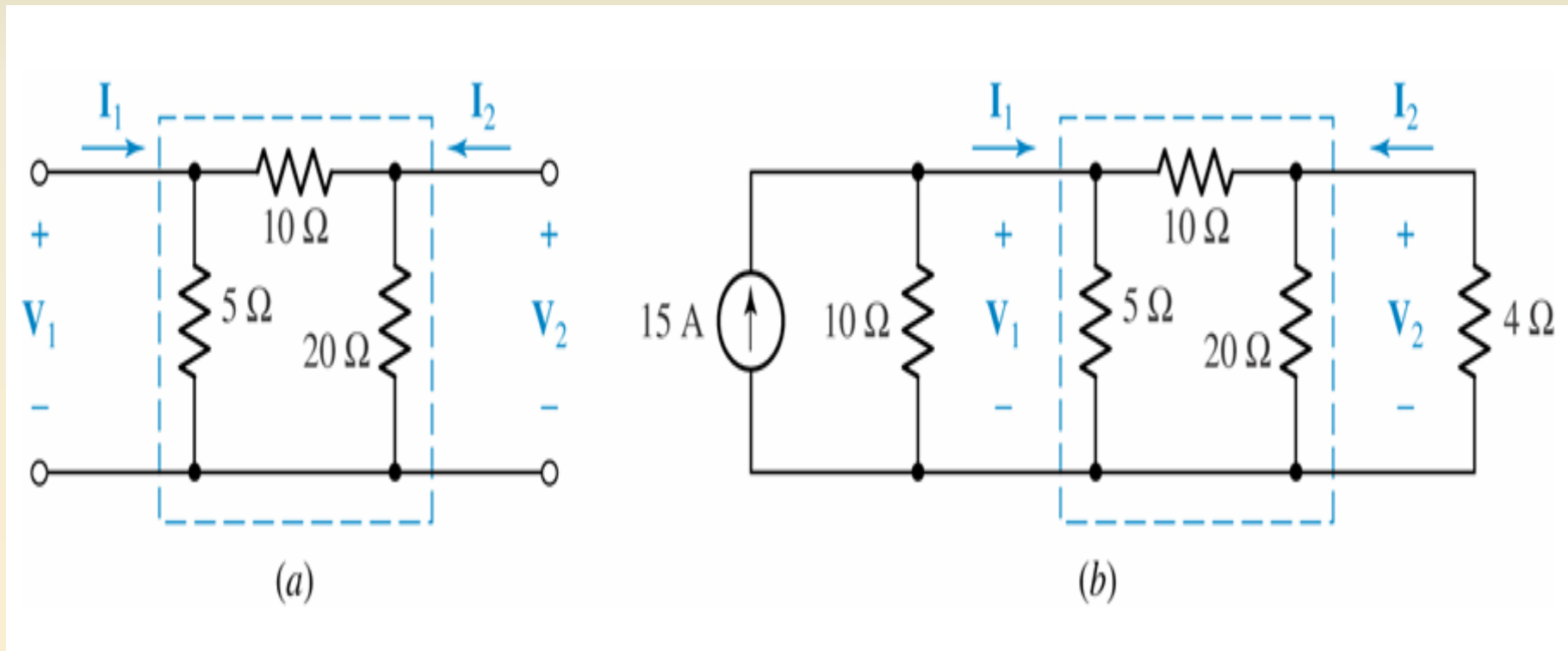Ex.: Find the four short-circuit admittance parameters for the resistive two-port shown below in (a).



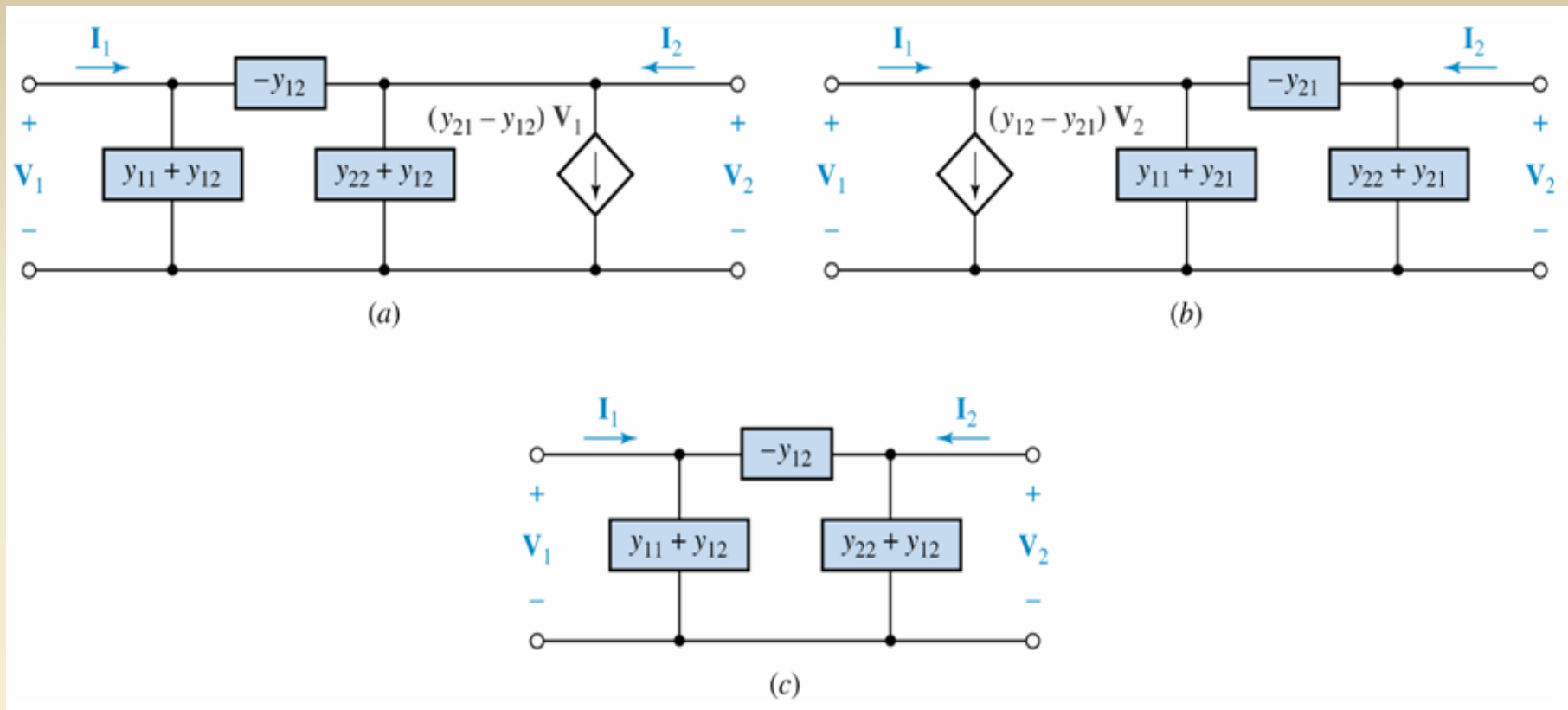


(a, b) Two-ports which are equivalent to any general linear two-port. The dependent source in part a depends on V_1 , and that in part b depends on V_2 . (c) An equivalent for a bilateral network.

W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.

Copyright ©2002 McGraw-Hill. All rights reserved.

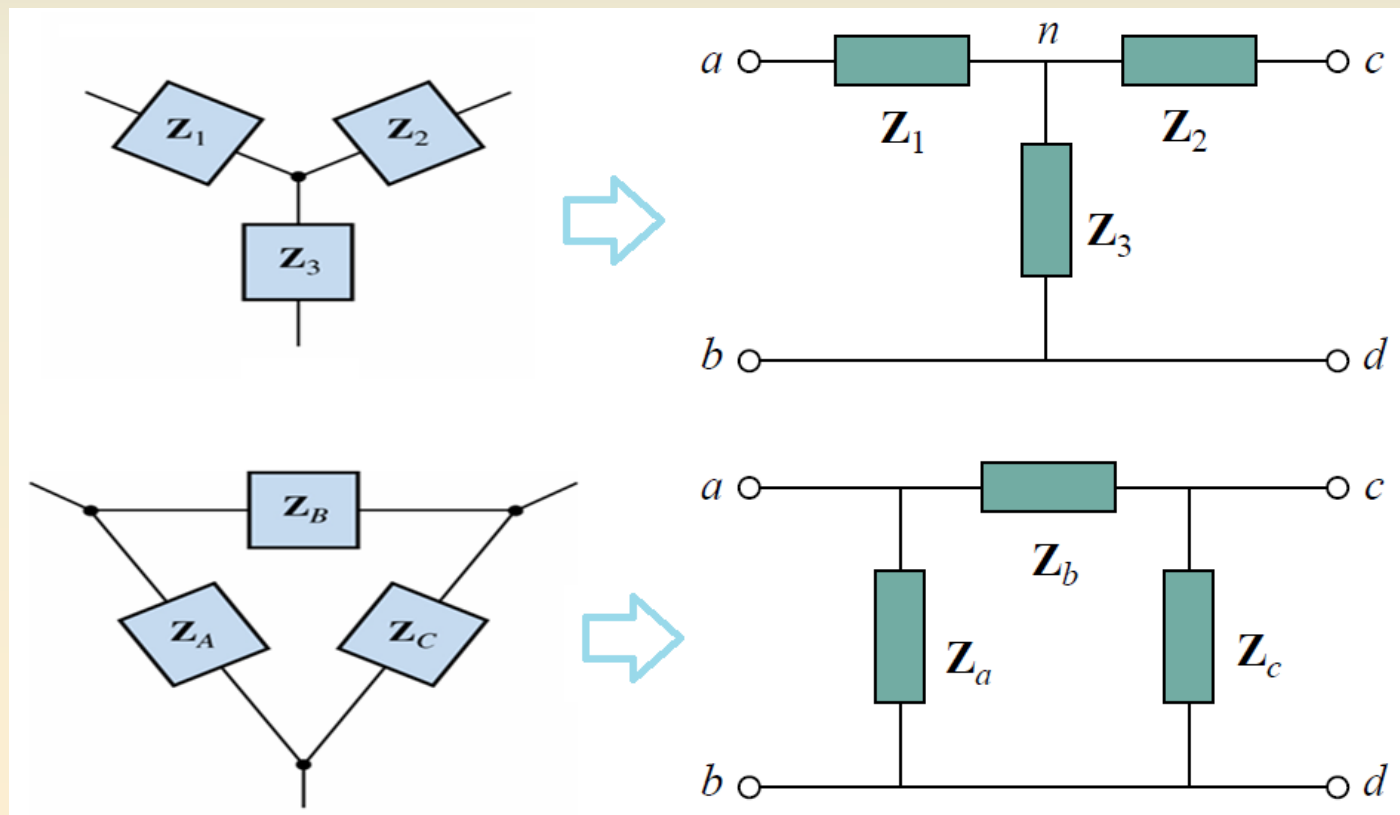
The three-terminal Δ network (a) and the three-terminal Y network (b) are equivalent if the six impedances satisfy the conditions of the Y- Δ transformation.




W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.

Copyright ©2002 McGraw-Hill. All rights reserved.

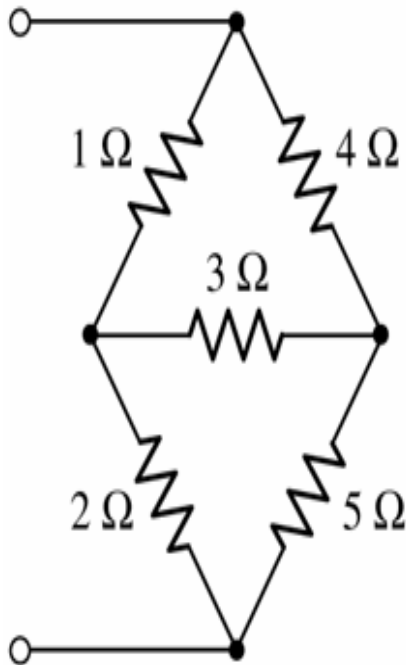
Find the input resistance of the circuit shown in (a).




(a)

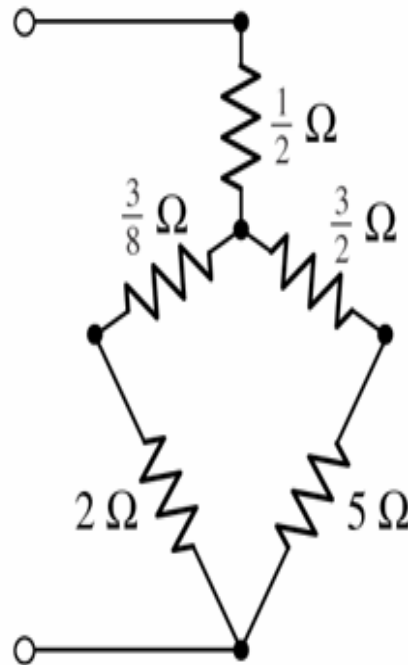

(b)

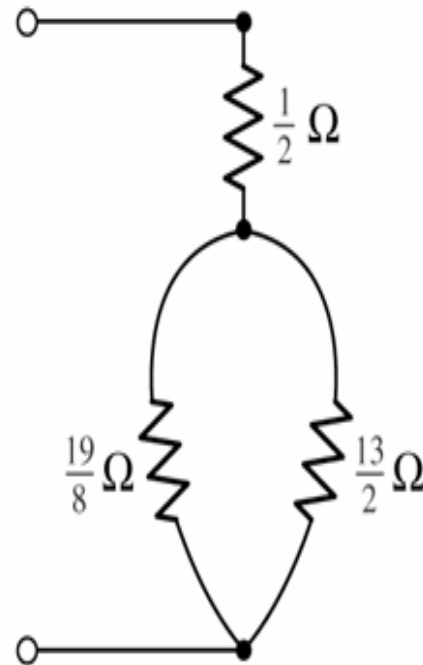

(c)

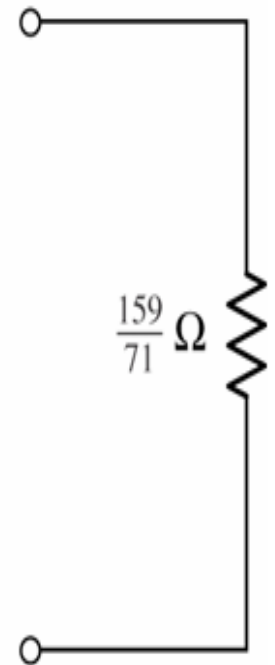

(d)

Ejo: Parámetros “h” o híbridos:

TRANSISTOR AMPLIFIER

Figure 17.9-1 shows the small signal equivalent circuit of a transistor amplifier. The data sheet for the transistor describes the transistor by specifying its h parameters to be

$$h_{ie} = 1250 \, \Omega, \quad h_{oe} = 0, \quad h_{fe} = 100, \quad \text{and} \quad h_{re} = 0$$

The value of the resistance R_c must be between $300 \, \Omega$ and $5000 \, \Omega$ to ensure that the transistor will be biased correctly. The small signal gain is defined to be

$$A_v = \frac{v_o}{v_{in}}$$

The challenge is to design the amplifier so that

$$A_v = -20$$

(There is no guarantee that these specifications can be satisfied. Part of the problem is to decide whether it is possible to design this amplifier so that $A_v = -20$.)

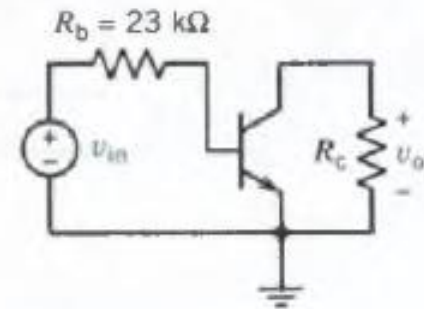


FIGURE 17.9-1 A transistor amplifier.


Describe the Situation and the Assumptions

1. R_c must be between $300\ \Omega$ and $5000\ \Omega$.
2. The transistor is represented by h parameters. Figure 17.9-1a shows that the transistor can be configured to be a two-port network and represented by h parameters. Figure 17.9-2b shows an equivalent circuit for the transistor. This equivalent circuit is based on the h parameters. For this particular transistor, the values of the h parameters are

$$h_{ie} = 1000\ \Omega, \quad h_{oe} = 0, \quad h_{fe} = 100, \quad \text{and} \quad h_{re} = 0$$


Because

$$\frac{1}{h_{oe}} = \infty$$

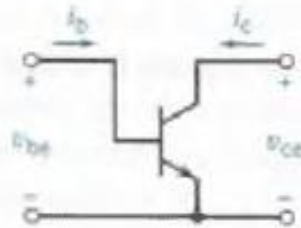


$$\begin{bmatrix} h_{ie} & h_{re} \\ h_{fe} & h_{oe} \end{bmatrix} \begin{bmatrix} i_b \\ v_{ce} \end{bmatrix} = \begin{bmatrix} v_{be} \\ i_c \end{bmatrix}$$

(a)

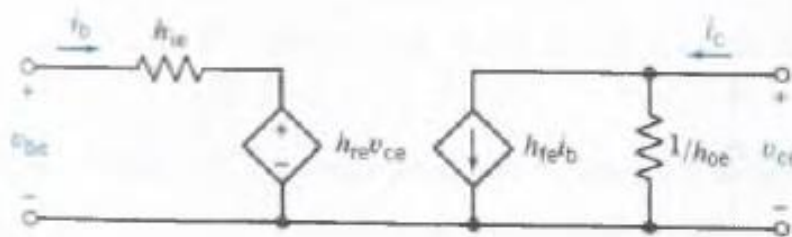

(b)

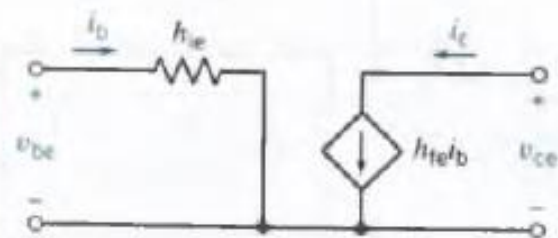

(c)

FIGURE 17.9-2 (a) Using h parameters to describe a transistor. (b) An equivalent circuit. (c) A simplified equivalent circuit for $h_{re} = 0$ and $h_{oe} = 0$.

the resistor at the right side of the equivalent circuit is an open circuit. Because

$$h_{re} = 0$$

the dependent voltage source is a short circuit. Figure 17.9-2c shows the equivalent circuit after these simplifications are made.

3. The voltage gain must be $A_v = -20$.

State the Goal

Select R_c so that $A_v = -20$.

Generate a Plan

Replace the transistor in Figure 17.9.1 by the equivalent circuit in Figure 17.9-2c. Analyze the resulting circuit to obtain a formula for the voltage gain, A_v . This formula will involve R_c . Determine the value of R_c that will make $A_v = -20$. If this value of R_c is between $300\ \Omega$ and $5000\ \Omega$, the amplifier design is complete. On the other hand, if this value of R_c is not between $300\ \Omega$ and $5000\ \Omega$, the specifications cannot be satisfied.

Act on the Plan

Figure 17.9-3 shows the amplifier after the transistor has been replaced by the equivalent circuit. Applying Ohm's law to R_c gives

$$v_o = -R_c 100 i_b$$

where the minus sign is due to reference directions. Next, apply KVL to the left mesh to get

$$v_{in} = 23,000 i_b + 1000 i_b$$

Then

$$A_v = \frac{v_o}{v_{in}} = \frac{-100 R_c}{24,000}$$

Finally, set $A_v = -20$, obtaining

$$-20 = \frac{-100 R_c}{24,000}$$

Now solve for R_c to determine

$$R_c = 4800 \Omega$$

Verify the Proposed Solution

First, the resistance $R_c = 4800 \Omega$ is indeed between 300Ω and 5000Ω . Second, the gain of the circuit shown in Figure 17.9-3 is

$$\frac{v_o}{v_{in}} = \frac{-h_{fe} R_c}{R_b + h_{ie}} = -\frac{100 \times 4800}{23,000 + 1000} = -20$$

Therefore, both specifications have been satisfied.


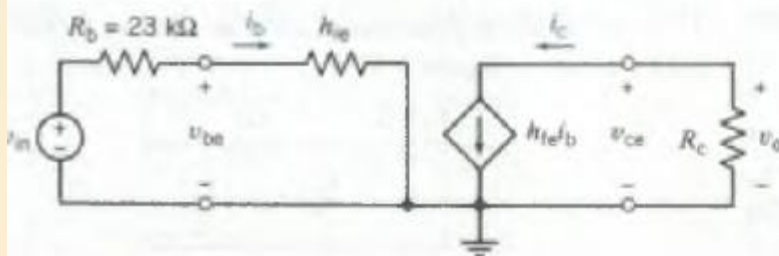
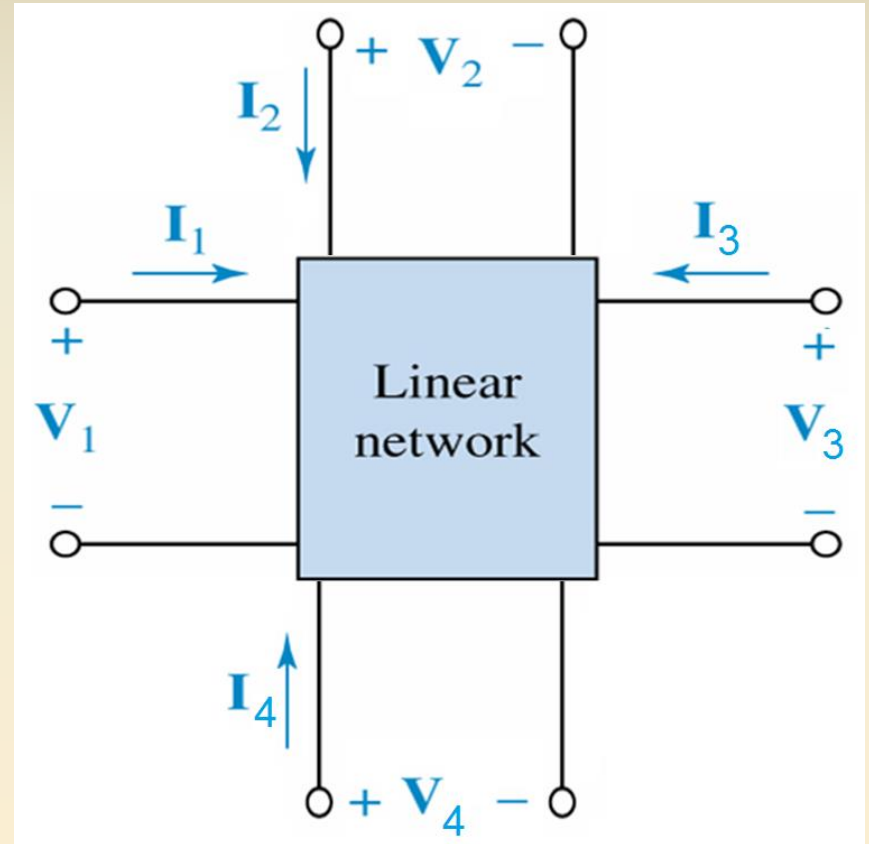


FIGURE 17.9-3 An equivalent circuit for the transistor amplifier.

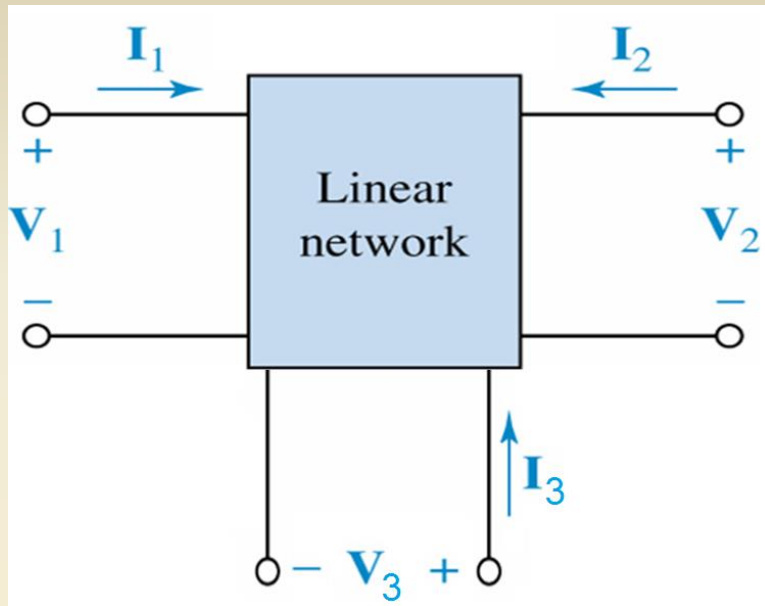Tarea: Resolver para redes Tripuertos y Cuadripuertos



$$\begin{bmatrix} Q_1 \\ Q_2 \\ \dots \\ Q_n \end{bmatrix} = \begin{bmatrix} K_{11} & K_{12} & \dots & K_{1n} \\ K_{21} & K_{22} & \dots & K_{2n} \\ \dots & \dots & \dots & \dots \\ K_{n1} & K_{n1} & \dots & K_{nn} \end{bmatrix} \begin{bmatrix} P_1 \\ P_2 \\ \dots \\ P_n \end{bmatrix}$$